

# Elec 422: VLSI Design I

Rice University

Spice Analysis of PseudoNmos and Static Complementary CMOS Circuits

## Spice

Examples of spice usage are located on OwlNet in /home/cavallar/demo, in the subdirectories cmos\_buffer (for static complementary buffer) and pseudonmos\_buffer (for pseudonmos buffer). Different ratios are presented for both experiments. The basic experiment file is:

```
*
* Elec422 SPICE EXPERIMENT TEMPLATE;
* -----

* Set BASIC VOLTAGE levels
vdd <Vdd> <GND> dc 5
* set substrate voltages : P-sub = Vdd; N-sub = GND
vs1 <CMOSP> <Vdd> dc 0
vs2 <CMOSN> <GND> dc 0

* -----

* Set Circuit Input which will change, for example a:
* input pulse between node and GND (initially 0 ) of:
* pulse (init_value pulse_value delay rise_time fall_time pulse_width period)
vin <input> <GND> 0 pulse(0 5 0ns 0.1ns 0.1ns 9.8ns 20ns)

* -----

* Do analysis: give increments and total time for analysis.
.tran .1ns 40ns
*
*
* If running in batch mode spice -b, then ascii plots are made
* Plot Voltages, for example a, sum, cout
.plot tran v(<input>) v(<output>) v(<outload>)


.end
```

PSEUDO-NMOS

$\frac{1}{2}$  RATIO  $\frac{PULLUP}{PULLDOWN}$


$$PULLUP = \frac{2}{6}$$

$$PULLDOWN = \frac{2}{3}$$

 

NOTE: LACK OF  
FULL VOLTAGE SWING.


PN  $\frac{1}{2}$  RATIO

 

nS

1hb


PSEUDO-NMOS  $\frac{4}{1}$  RATIO

 


PN  $\frac{4}{1}$  RATIO

--- v(5)      --- v(4)  
--- v(6)

 Note: slower circuit response,  
especially slow rise times



 
PSEUDO - NMOS  $\frac{1}{\frac{1}{4}} = \frac{4}{1}$  RATIO



PSEUDO-NMOS  $\frac{4}{1}$  RATIO  
WIDE

--- v(5)      --- v(4)  
--- v(6)

Note: More balanced rise and fall times.

 

---

# **DIGITAL CMOS CIRCUIT DESIGN**

by

**Marco Annaratone**  
Carnegie-Mellon University  
Pittsburgh, Pennsylvania



**KLUWER ACADEMIC PUBLISHERS**  
Boston / Dordrecht / Lancaster



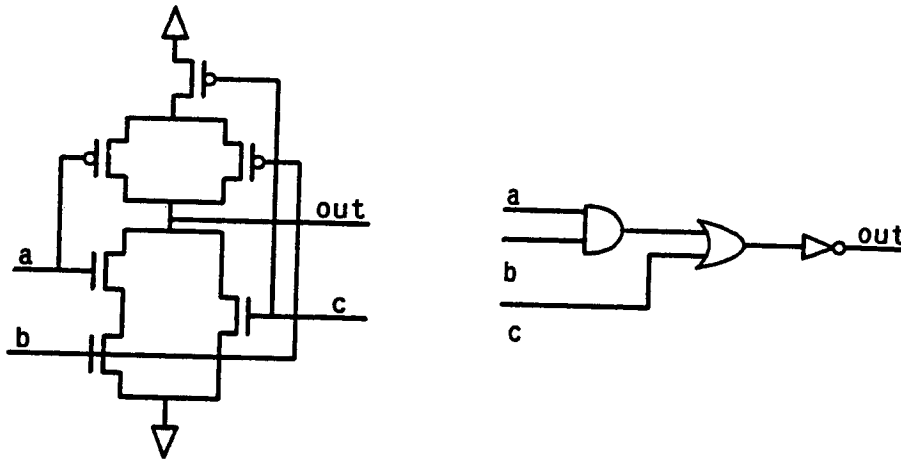


Figure 4-1: AOI implemented in complementary logic (left) and its representation in terms of basic gates.

#### 4.1.2. nMOS-like Logic

The nMOS-like implementation of an AOI gate is shown in Fig. 4-2. Fig. 4-2(a) shows the n-channel based version, while Fig. 4-2(b) shows the p-channel based version. Each input is connected to the gate of only one device — instead of two as in complementary logic. Moreover, if the gate has  $n$  inputs, only  $(n+1)$  devices are necessary. This logic occupies less area than complementary logic. Concerning circuit speed, nMOS-like logic was faster than complementary logic [12] in the early days of CMOS technology, when the gate capacitance of the MOS transistor was indeed a limiting factor. With fabrication processes of about  $3\mu\text{m}$  and smaller, this is no longer true. Although the input capacitance is smaller than in complementary logic, because the input is connected to only one device, the pull-up section in Fig. 4-2(a) is a p-channel transistor used as a resistor, and the current which is delivered suffers from energy dissipation. We conclude that the two effects — decreased input capacitance but also decreased driving capability — balance each other.

 


Figure 4-2: CMOS, nMOS-like AOI gates using n-channel devices (a) or p-channel devices (b).

nMOS-like logic is a *ratioed* logic. The pull-up and pull-down sections have to satisfy a certain range of ratios, otherwise the output voltage might not be able to switch the next gate(s) and/or the noise margin might be adversely affected, as shown in Figs. 4-4 and 4-5. Fig. 4-4 shows the input to an nMOS-like inverter (see Fig. 4-3 (left)) and six output curves. These curves refer to the same inverter with different pull-up|pull-down ratios. The two transistors have the same width, and the inverter drives a load of  $10^{-3}$  pF. Curve 1 refers to the inverter with a pull-up|pull-down ratio of 1|1; curve 2 refers to the inverter with a pull-up|pull-down ratio of 2|1 (i.e., the p-channel device is twice as long as the n-channel device and both have the same width), and so on. Ratios of 1|1 and 2|1 are unacceptable. Besides providing poor noise margin, the output low level is close to 0.6V. When this output is connected to similar nMOS-like gates, it keeps the n-channel device(s) weakly off and drastically increases static power dissipation. In order to improve the noise margin and strongly turn off n-channel transistors in other gates, a ratio of either 4|1 or 5|1 is normally used. This is done at the expense of output rise-time, which increases when the ratio increases.



Figure 4-3: Inverter configurations for nMOS-like logic.

 


Figure 4-4: nMOS-like inverter of Fig. 4-3 (left): input signal (bold) and six output signals for different pull-up|pull-down ratios.

 


Figure 4-5: nMOS-like inverter of Fig. 4-3 (right): input signal (bold) and six output signals for different pull-up|pull-down ratios.

Fig. 4-5 shows the input signal to an inverter with a “complementary” configuration (see Fig. 4-3 (right)) and six output waveforms. The gate of the n-channel device is connected to  $V_{dd}$ , and the input signal is connected to the gate of the p-channel device. Both transistors have the same length. Curve 1 shows the output waveform for a pull-up|pull-down ratio of 1|1; curve 2 refers to a pull-up|pull-down ratio of 1|2 (i.e., the n-channel device is twice as wide as the p-channel transistor), and so on. Note that performance degradation is much more significant, and a ratio of 6 has to be considered the minimum requirement. Therefore, only a logic like the one shown in Fig. 4-2(a) is usually implemented.


Finally, as in nMOS design, NOR-based gates are always preferred to NAND-based gates, because a NAND gate in this logic requires a long p-channel device to satisfy the necessary pull-up|pull-down ratio, making the layout more complex and slowing down the circuit. The most serious drawback of this logic is that a direct path between  $V_{dd}$  and  $V_{ss}$  exists when the input is high in the circuit in Fig. 4-3 (left). nMOS-like logic suffers from static power dissipation.

There are some applications where this logic can be useful, such as decoders with severe area limitations and no clock availability. As a general guideline, this logic can be implemented when power dissipation is not a major concern, circuit density is of fundamental importance, and no clock is available — either because there is no clock or because it cannot be used. Finally, note that the difference in power dissipation between nMOS-like and complementary logic *decreases* with higher frequency of utilization of the complementary gates, because dynamic power dissipation is proportional to the frequency of operation of the circuit, as shown in Eq. (2-23).

STATIC  
COMP.

BASIC

 
$$\text{RATIO} = \frac{\frac{2}{3}}{\frac{2}{3}} = 1$$



STATIC BASIC  
COMP

RATIO = 1

--- v(5)      --- v(4)  
--- v(6)

 


STATIC  
COMP

WIDE  
PULLUP

$$\text{RATIO} = \frac{\frac{2}{6}}{\frac{2}{3}} = \frac{1}{2}$$

 Note: Preferred  
Inverter ratio  
for more equal  
rise and fall  
times



Static Complementary CMOS with Wider Pullup P channel transistor to reduce pullup resistance and achieve more balanced rise and fall times.

Note: Faster Rise Time with Ratio = 1/2

