

ELEC 243
Problem Set 8
Homework Section
Due: March 20, 2015

H8.1 Work Problem 4.8 in K&I.

H8.2 Work Problem 4.11 in K&I.

H8.3 Work Problem 4.21 in K&I.

H8.4 Write the following as phasors:

(a) $i(t) = 3 \cos(\omega t + 45^\circ)$


(b) $x(t) = X_M \sin(\omega t)$

(c) $v_1(t) = -6 \cos(\omega t - 30^\circ)$

(d) $v_2(t) = 5 \sin(\omega t + 10^\circ)$

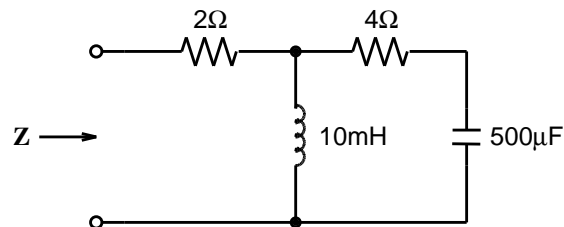(e) $v(t) = v_1(t) + v_2(t)$ (where v_1 and v_2 are given in parts (c) and (d))

H8.5 In the network below, find \mathbf{Z} at a frequency of 60 Hz.



H8.6 Find the impedance of the circuit below if the time-domain functions represented by the phasors \mathbf{V} and \mathbf{I} are

(a) $v = -30 \cos 2t + 16 \sin 2t$ V, $i = 1.7 \cos(2t + 20^\circ)$ A.

(b) $v = \text{Re}[j e^{j2t}]$ V, $i = \text{Re}[(1 + j)e^{j(2t+30^\circ)}]$ mA.

(c) $v = a V_m \cos(\omega t + \theta)$ V, $i = V_m \cos(\omega t + \theta - \alpha)$ A.

